



KEMENTERIAN PENGAJIAN TINGGI



e-Book

### ELECTRICAL ENGINEERING DEPARTMENT

**ELECTRONIC CIRCUITS** 





AUTHOR ANIRA BINTI ABDUL RASHID GAURI A/P BIRASAMY



## DC POWER SUPPLY

### AUTHOR Anira Binti Abdul Rashid Gauri A/p Birasamy

Copyright © 2023

All rights reserved. No part of this publication may be reproduced, distributed, or transmitted in any form or by any means, including photocopying, recording, or other electronic or mechanical methods, without the prior written permission of the publisher, except in the case of brief quotations embodied in critical reviews and certain other noncommercial uses permitted by copyright law. For permission requests, write to the publisher at the address below.

ISBN: 978-967-2740-59-9


Politeknik Tuanku Sultanah Bahiyah (PTSB) Kulim Hi-Tech Park, 09090 Kulim, Kedah. https://ptsb.mypolycc.edu.my

### Thanks to our family and colleagues at Electrical Engineering Department, Politeknik Tuanku Sultanah Bahiyah for being the support team to complete this e-book. Last but not least we also thank you to the "PTSB Team E- Book" and technical

team for guiding us in completing this e-book.
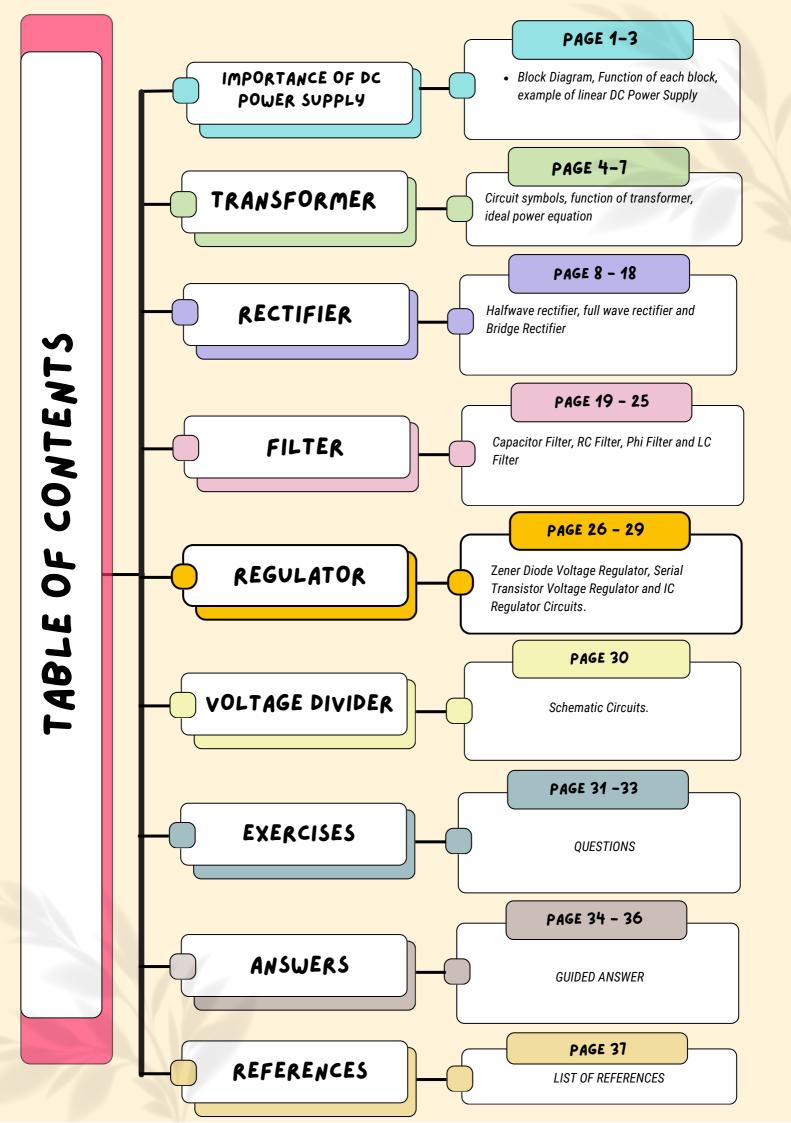
### SYNOPSIS

"Discover the essentials of DC Power Supply in this dedicated eBook crafted for third-semester students diving into electronic circuits. Covering transformers, rectifiers, filters, and voltage regulators, this guide simplifies complex concepts with clear explanations and practical examples. Tailored for easy understanding, it's an accessible resource packed with real-world applications, enabling students to grasp and apply DC power supply fundamentals effectively."



## IMPORTANCE OF DC POWER SUPPLY;



Most electric equipment requires DC voltage.

Dry cells unable to accommodate the needs of electrical equipments.




Power supplied to the house in AC but electrical equipment needs DC voltage.


# BLOCK DIAGRAM

Block Diagram	Voc	Transformer		Rectifier		Filter		Regulator	]	Voltage Divider	Yae
Output Voltages	¥₀ X₀		¥. Av		¥• 		↓ ↓ ↓		¥¤ ↓		

Fig 1 : Block diagram



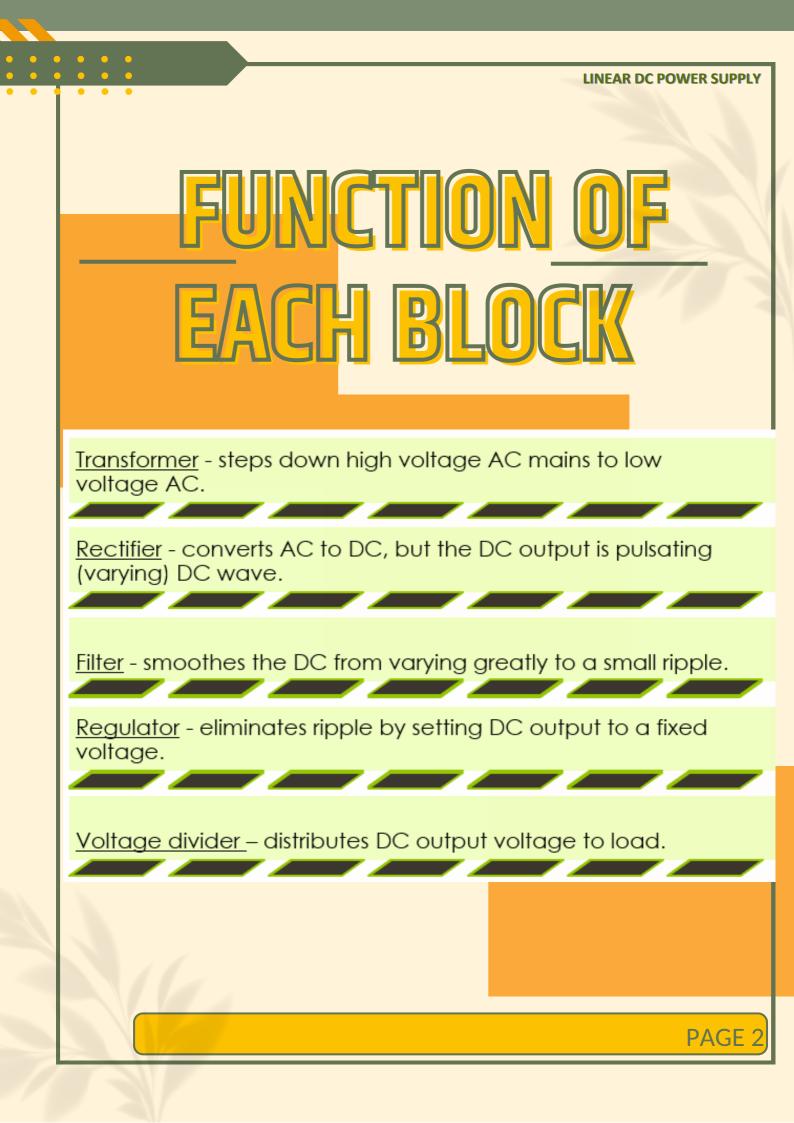

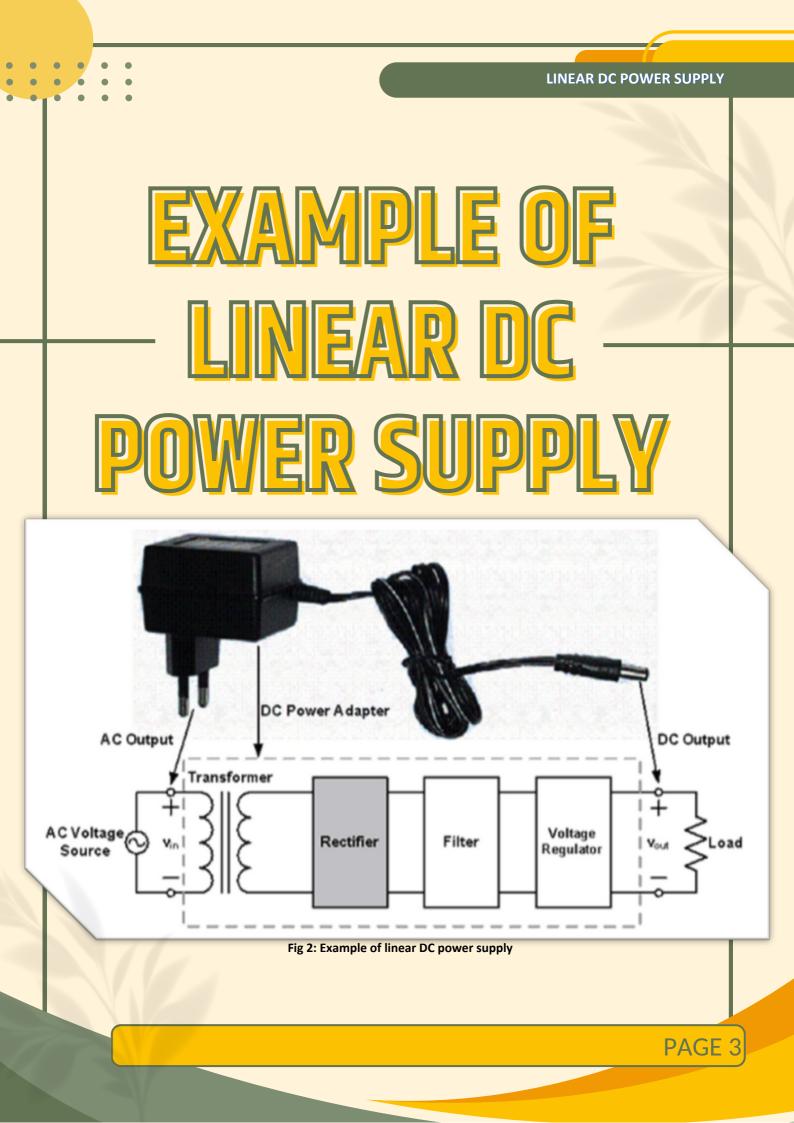


# TRANSFERMERS


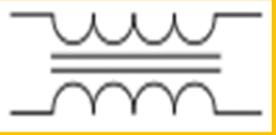
## <u>CIRCUIT SYMBOLS</u>

Transformer with two windings and iron core as in figure 4.



LINEAR DC POWER SUPPLY

Fig 4: Transformer with two windings and iron core.

Step-down or step-up transformer. The symbol shows which winding has more turn but not usually the exact ratio as in figure 5.



Fig 5:Step-down or step-up transformer.



## TRANSFORMER

TRANSFORMER

Transformers convert AC electricity from one voltage to another with little loss of power.

> Transformers work only with AC and this is one of the reasons why mains (wall socket) electricity is AC.

5

Step-up transformers increase voltage, step-down transformers reduce voltage.

Most power supplies use a step-down transformer to reduce the dangerously high mains voltage (240V in Malaysia) to a safer low voltage.

PAGE 5

The input coil is called the primary and the output coil is called the secondary.

There is no electrical connection between the two coils, instead they are linked by an alternating magnetic field created in the softiron core of the transformer.

The two lines in the middle of the circuit symbol represent the core.

6

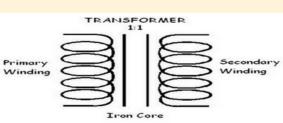


Fig 6:Transformer.

## TRANSFORMER

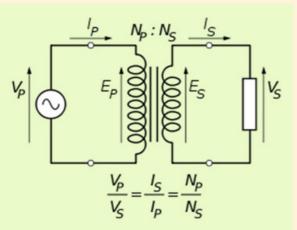


Fig 7:Transformer.

Vp ; Primary (input) Voltage

Np ; Number of turns on primary coil

Ip; Primary (input) Current

Vs; Secondary (output) Voltage

Ns; Number of turns on secondary coil

Is; Secondary (output) current

A step-down transformer has a large number of turns on its primary (input) coil which is connected to the high voltage mains supply.

A small number of turns on its secondary (output) coil to give a low output voltage.

If the secondary coil is attached to a load that allows current to flow, electrical power is transmitted from the primary circuit to the secondary circuit

Ideally, the transformer is perfectly efficient; all the incoming energy is transformed from the primary circuit to the magnetic field and into the secondary circuit as figure 7.

If this condition is met, the incoming electric power must equal the outgoing power:

 $P_{in} = P_{out}$  $I_p V_p = I_s V_s$  $\frac{V_p}{V_s} = \frac{I_s}{I_p}$ 

Ip = primary (input) current Is = secondary (output) current

LINEAR DC POWER SUPPLY

PAGE

PAGE

## TRANSFORMER



Note that as voltage is stepped down, current is stepped up. If the voltage is increased, then the current is decreased by the same factor.



An ideal transformer would have no energy losses, and would be 100% efficient.



In practical, transformers waste very little power so the power out is (almost) equal to the power in. Transformers energy is dissipated in the windings, core, and surrounding structures. Larger transformers are generally more efficient, and those rated for electricity distribution usually perform better than 98%.



PAGE





Conversion of alternating current (or voltage) into direct current (or voltage) is called rectification.

A diode is well-suited for this job because it only conducts when forward-biased. The component at figure 8 is bridge rectifier.

**Types Of Rectifiers :** 

- Half-wave rectifier
- Full-wave rectifier
- Bridge rectifier




HALF-WAVE RECTIFIER


An a.c voltage is applied to a single diode connected in series with a load resistor, RL. the schematic diagram is show in figure 9.


A single diode can be used as a rectifier but this produces half-wave varying DC which has gaps when the AC is negative.

It only uses the positive (+) parts of the AC wave to produce half-wave varying DC.

Schematic diagram :

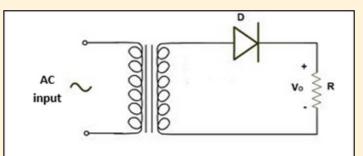

 

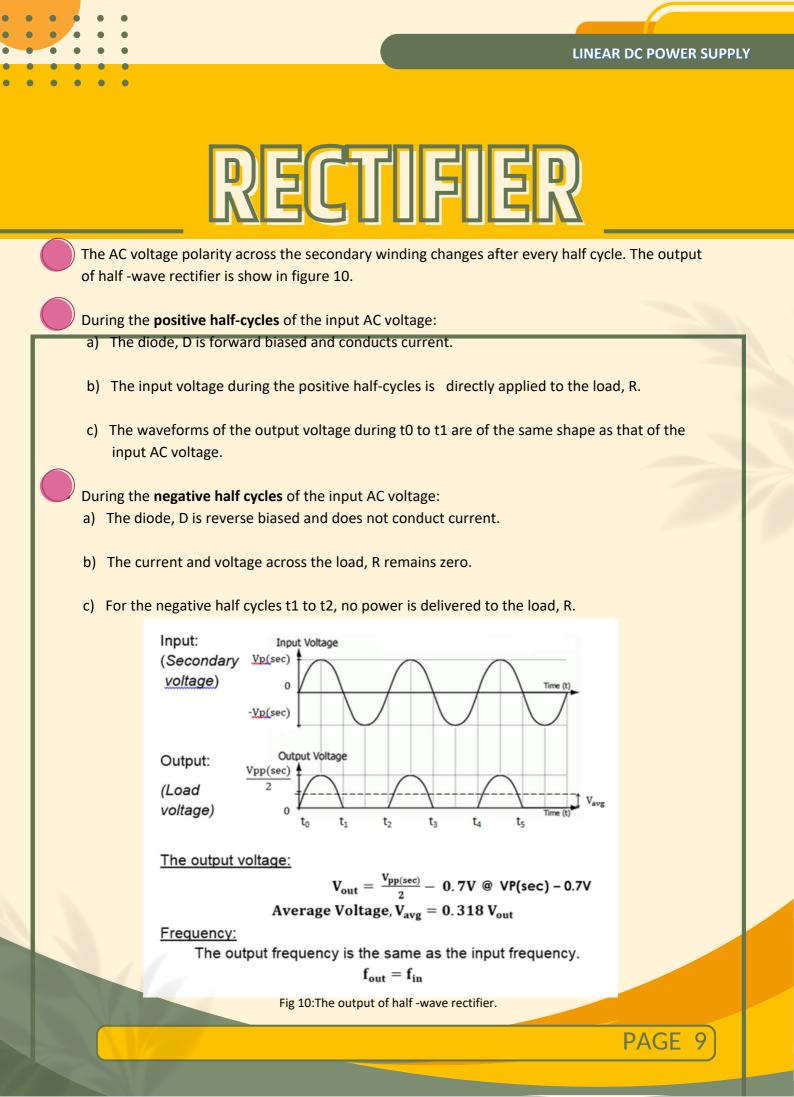



### **FULL-WAVE RECTIFIER**

- The full-wave rectifier circuit using two diodes and a center-tapped transformer, which usually taken as the ground or zero voltage reference point as show in figure 11.
- It is called a full-wave rectifier because it uses the entire AC wave (both positive and negative sections).
- There are two main types of full wave rectifiers:
  - a) Center-tapped full-wave rectifierb) Bridge rectifier
- a) Center-tapped full-wave rectifier :
- The figure 12 shows that two diodes connected to the secondary of a centertapped transformer can form a full-wave rectifier that allows both half-cycles of the AC waveform to contribute to the DC making it smoother than a half-wave rectifier
- Grounded center tapped results in ½ secondary voltage reaching the load.
- The purpose of center-tapped transformer is to get two a.c. output with the same value but in inverse phase. The input and output voltage of full wave show in figure 13.



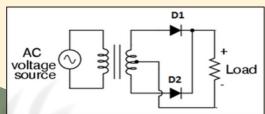


Fig 12:Circuit diagram of full -wave rectifier.

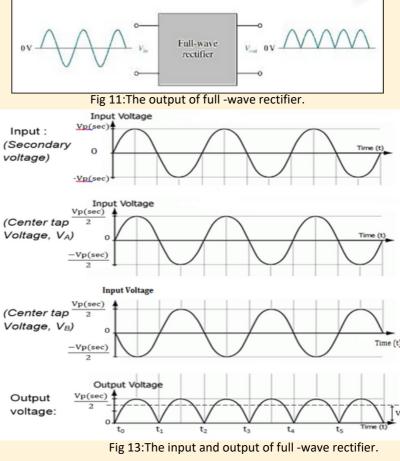

PAGE

10

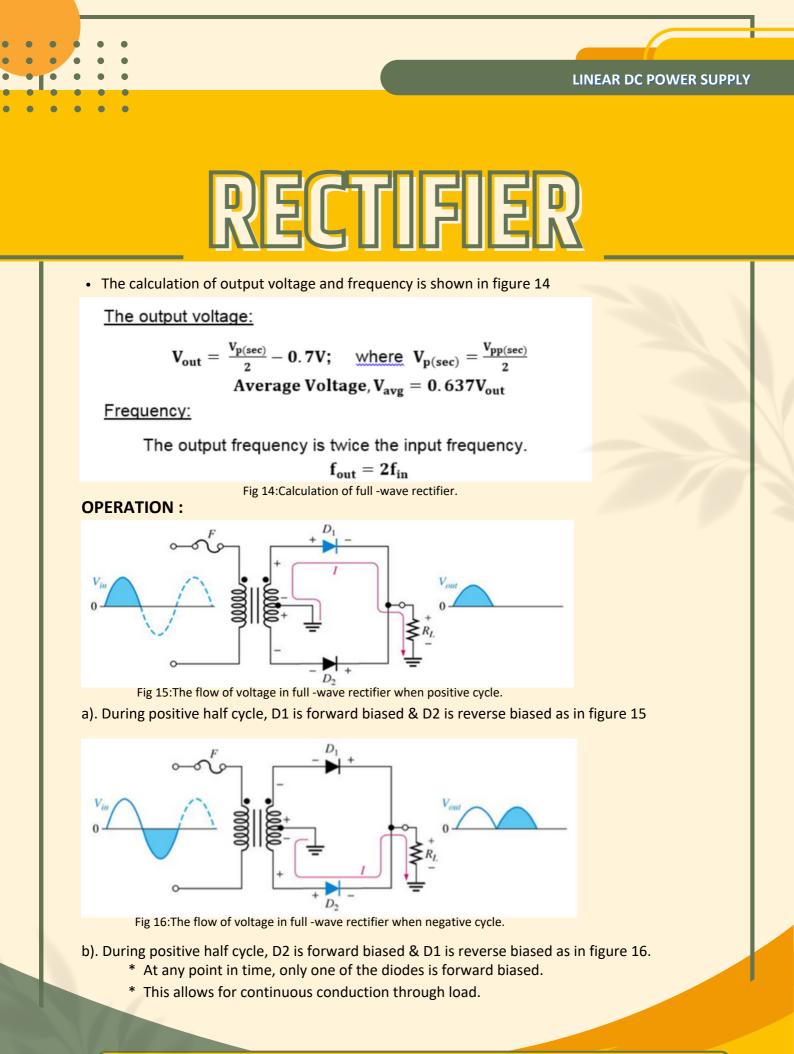

PAGE 11

PAGE 12



### b) Bridge rectifier :




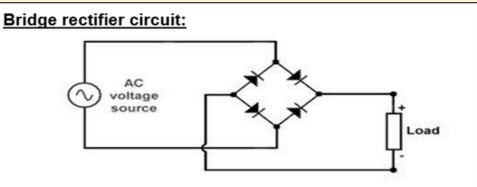


Fig 17:Bridge rectifier circuit diagram.

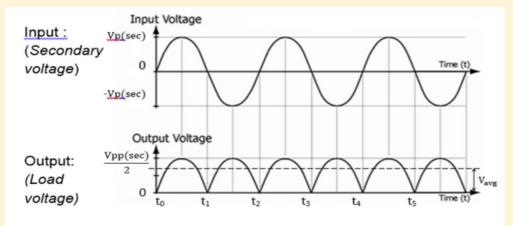A bridge rectifier can be made using four individual diodes as show in figure 17 and the input and output voltage in figure 18.



The output voltage:


$$V_{out} = rac{V_{pp(sec)}}{2} - 1.4V$$
  
Average Voltage,  $V_{avg} = 0.637 \, V_{out}$ 

Frequency:

The output frequency is twice the input frequency.

$$f_{out} = 2f_{in}$$


Fig 18:The input and output of bridge rectifier.

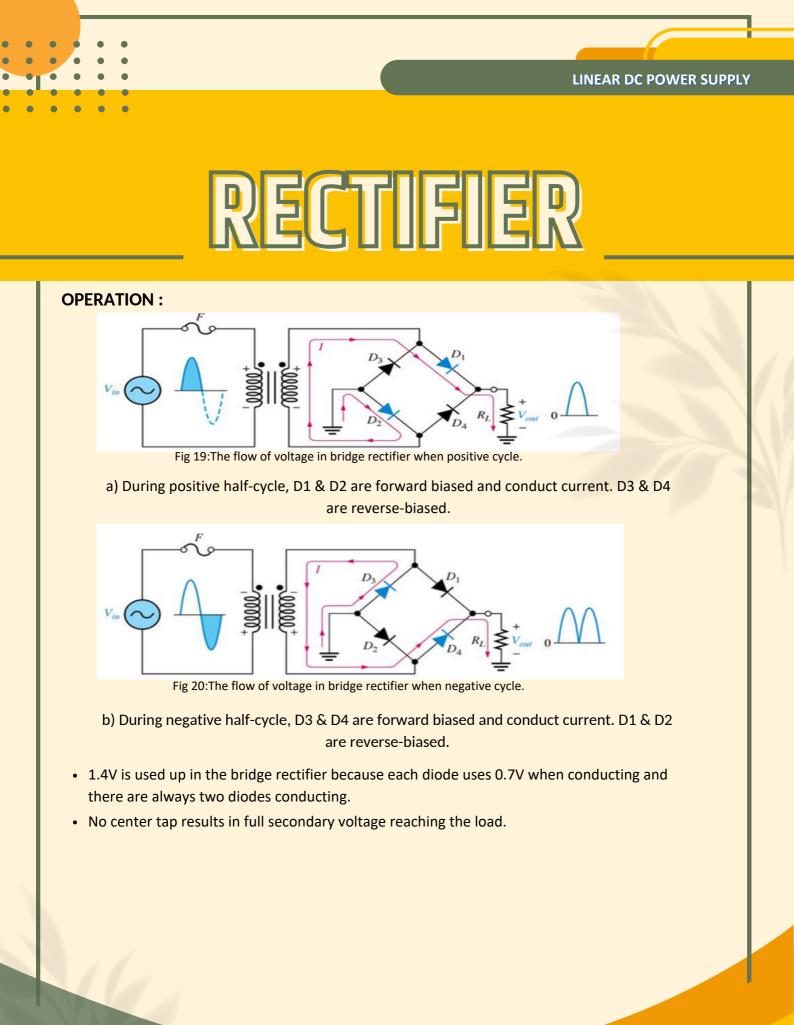

PAGE 13

## RECTIFIER

### Bridge Rectifier IC

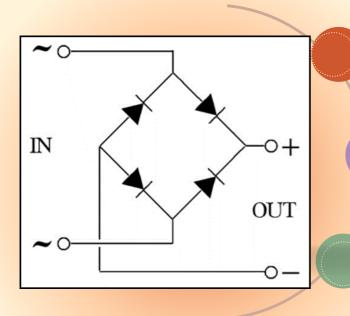

Bridge rectifier is also available in special packages containing the four diodes required.

Bridge Rectifiers typically marked with an "BR" on a circuit board.

The various case designs are shown figure 21.



Fig 21:Examples of bridge rectifier




**PAGE 15** 



Table 1: Summary of rectifier

• •

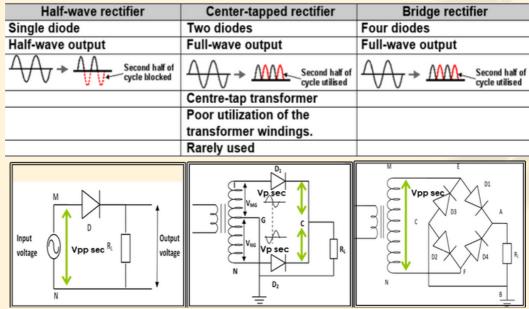

,	Halfwave rectifier	Fullwave Rectifier	Bridge rectifier		
	Thuj wave recujier	Failwave Kectijier	Drugerecujier		
No. of diodes	1	2	4		
Output Voltage	Vo = Vp sec - 0.7V	$V_0 = V_{p sec} - 0.7V$	Vo = Vp sec - 1.4V		
(V <sub>o</sub> )	** Vp sec = V2 x Vrms	2			
Average Voltage	$V_{avg} = V_0$	Vavg =	= <u>2Vo</u>		
(V <sub>avg</sub> )	π		π		
	or	or.			
	$V_{avg} = 0.318 V_o$	Vavg = 0	.636 V <sub>o</sub>		
Average Current	Iavg = <u>Vavg</u>	Iavg =	Vavg		
(I <sub>avg</sub> )	RL		RL		
	or	or.			
	$I_{avg} = I_m/\pi$	Iavg = 2	2Im/π		
Root mean		$V_{rms} = V_{p sec}$			
square voltage	ν2				
(Vrms)	or				
	Vrms = 0.707 Vp sec				
Output frequency	Same as input freq.	2 x in	put freq.		
		·			




PAGE 16


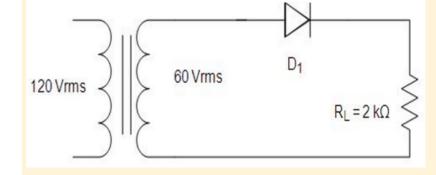
### Example 1:

A half wave rectifier build in 60 Vrms in the secondary of the transformer. Calculate:-



i. The output voltage. ii.Average voltage of the circuit

> Solution : i. Output voltage, Vo  $Vo = \frac{Vpp_{sec}}{2} - 0.7 \lor @ Vp_{sec} - 0.7 \lor$ From formula, Vp sec =  $\sqrt{2} \times Vrms$   $= \sqrt{2} \times 60$   $= 84.85 \lor$ Therefore, Vo =  $Vp_{sec} - 0.7 \lor$  = 84.85 - 0.7 $= 84.16 \lor$

ii. Average voltage, Vavg

$$Vavg = \frac{Vo}{\pi}$$
  
=  $\frac{84.16}{\pi} = 26.7 V$ 






### Example 2:

In a centre-tap full wave rectifier, load resistance is  $2K\Omega$ . The a.c. supply across the primary winding is 220V. Taking transformer turn ratio N1/N2 =  $\frac{1}{2}$  and neglecting diode resistance. Determine:i. Output voltage

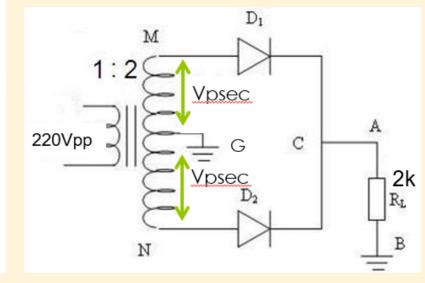- ii. Average voltage
- iii. Average current



### Solution :

i. Output voltage, Vo

$$Vo = \frac{Vp_{sec}}{2} - (0V)$$

neglecting diode resistance


To find *Vpp<sub>sec</sub>*:

$$\frac{v_p}{v_s} = \frac{Np}{Ns} \implies \frac{v_{p_{pri}}}{v_{p_{sec}}} = \frac{Np}{Ns}$$

$$\frac{110V}{Vp_{sec}} = \frac{1}{2} \qquad \Longrightarrow Vp_{sec} = (110V)(2) = 220V$$

So, Vo = 
$$\frac{220}{2} - 0V = 10V$$

ii. Average voltage, Vavg

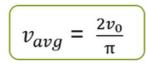

$$=\frac{(2)(220)}{\pi}=$$
140V

PAGE 17

### iii. Average current, lavg


$$I_{avg} = \frac{v_{avg}}{RL}$$
$$= \frac{140}{2K\Omega} = \underline{70mA}$$




### Example 3:

A full wave rectifier with a 120 Vrms sinusodial input had a load resistor of  $1K\Omega$ . If silicone diodes are employed, determine:-

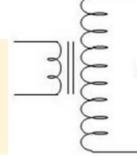- i. Average voltage available at the load.
- ii. Average current



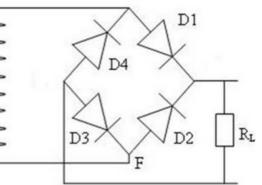

Solution :

i. Average voltage, Vavg

$$v_{avg} = \frac{2v_0}{\pi}$$

$$Vo = \frac{Vpp_{sec}}{2} - 1.4V @ Vp_{sec} - 0.7V$$

Vp sec =  $\sqrt{2} x Vrms$ 


$$Vp$$
 sec =  $\sqrt{2} \times 120$  = 169.7 V

<u>Vava</u> =  $\frac{(2)(168.3)}{\pi}$  = **<u>107.14V</u>** 

ii. Average voltage, <u>Vavg</u>

$$I_{avg} = \frac{V_{avg}}{RL}$$



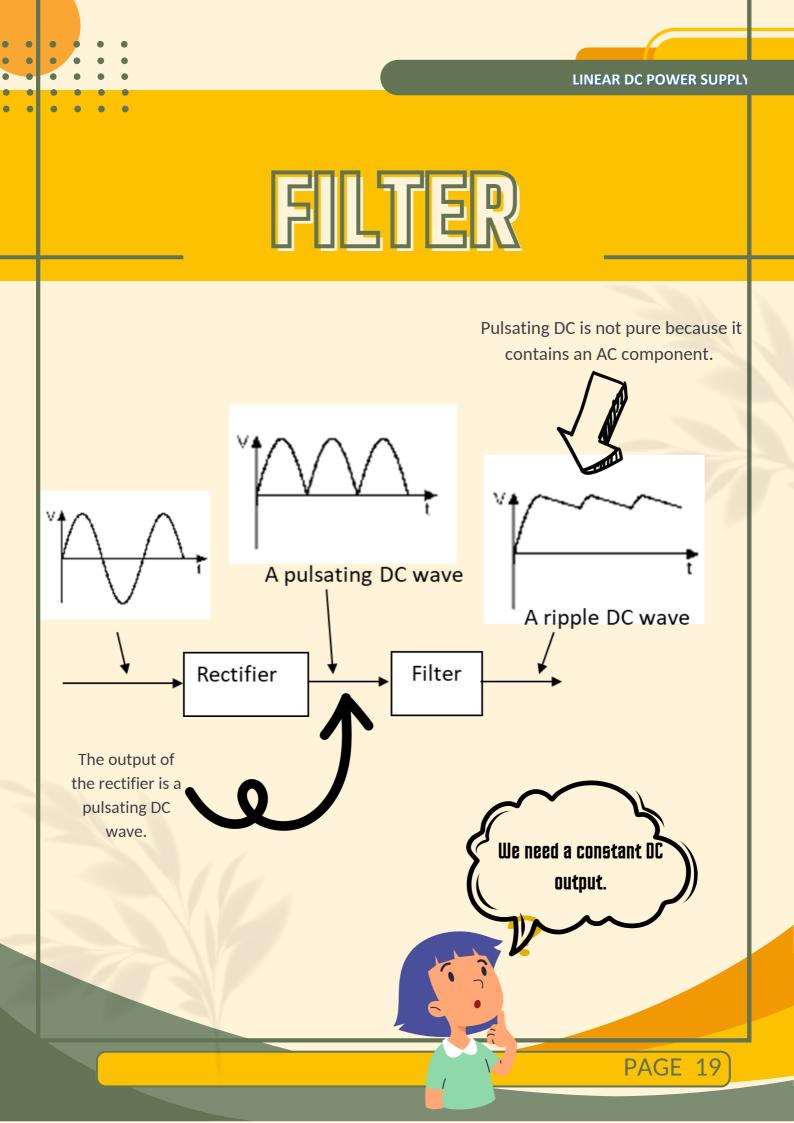



PAGE 20

## FILTER

The AC component in DC power supply is called ripple. Ripple is usually to be considered as unwanted effect.

**02** ຕຳຳ

01

 $\square$ 

Ripple is the small unwanted residual periodic variation of the direct current (DC) output of a power supply which has been derived from an alternating current (AC) source.

03 ₽

Filter is the circuit used to remove the ripple and produce a very smooth waveform.



05

To do this, we need to filter out the oscillations from the pulsating DC wave. Figure 2.2 show the The ripple output at (a) Half-wave and (b) Full-wave rectifier.

This is obtained with a diode and capacitor combination. The capacitor can more effectively reduce the ripple when the time between peaks is shorter.

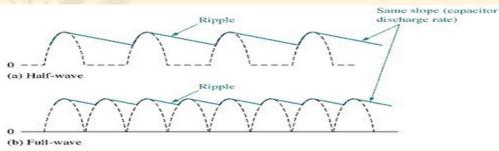


Fig 22:The ripple output at (a) Half-wave and (b) Full-wave rectifier



### **CAPACITOR FILTER**

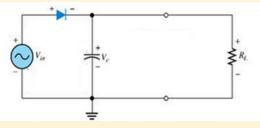


Fig 23:Capacitor Filter

- A capacitor is connected in parallel with a load resistance (RL) as in figure 23.
- Capacitor offers a low reactance to a.c components.
- Once charging, capacitor will store the charges until the current reach a complete cycle.

### **CAPACITOR FILTER (Operation)**

- Initial charging of capacitor (diode is forward-biased) happens only once when power is turned on as in figure 24.
- Currents from a rectifiers will cause a drop voltage across RL and charging the capacitor because they are connected in a parallel circuit.


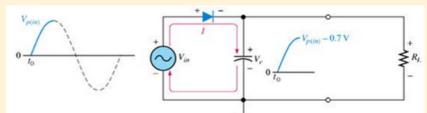


Fig 24:Initial charging of capacitor happens only once when power is turned on.

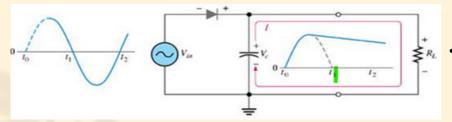

 The capacitor discharge through RL after peak of positive alteration when the diode is reverse-biased as in figure 25.

Fig 25:The capacitor discharge through RL.

- This discharging occurs during the portion of the input voltage indicated by solid curve.
- The input begins to decrease below its peak to OV, while the capacitor is begin to discharge.
- The discharging time is longer than decreasing the voltage to OV.





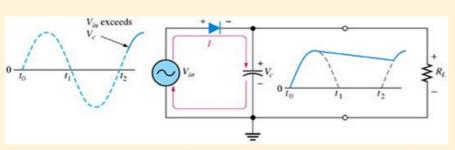


Fig 26:The capacitor charges back to peak of input when diode becomes forward-biased.

- The capacitor charges back to peak of input when the diode becomes forward-biased as in figure 26.
- This charging occurs during the portion of the input voltage indicated by the solid blue curve.
- Before completing the discharging process, another input voltage of the positive half-cycle charging the capacitor once again

PAGE

22

- The higher value of capacitor will remove ripple voltage more effective because the higher value of capacitor will take more times to discharge (Time constant longer) as in figure 27.
- Higher capacitor value, smaller ripple voltage.

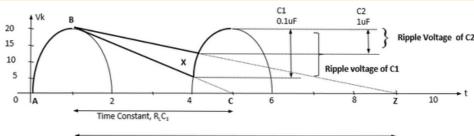
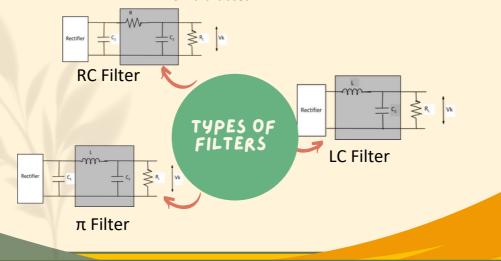


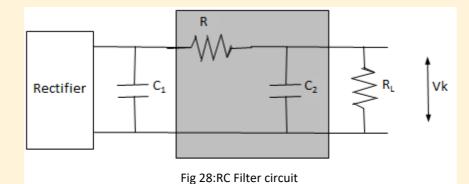


Fig 27:The capacitor charges back to peak of input when diode becomes forward-biased.



## FILTER

### a). RC FILTER



- RC filter is produced by placing a resistor (R) in series with the load, while a capacitor (C<sub>2</sub>) in parallel with the load, R<sub>L</sub>.
- In this circuit, the ripples have to be made to drop across the resistance (R) instead
  of the load resistance (RL).
- So, resistance value (R) is kept much larger than reactance of capacitor C<sub>2</sub> (Xc<sub>2</sub>).
- Typically, R is kept 10 times greater than Xc2; this means each section reduce the ripples by a factor of at least 10.
- C1 performs exactly the same function as it did in the single capacitor filter. It is used to reduce the percentage of ripple to a relatively low value.
- C2 act as a filter for the balance ripples.


#### The main disadvantages of R-C filter:

- Large voltage drops in the series resistor R (poor voltage regulation). DC output voltage across load, RL will also be diminished to a lower value.
- Power is wasted in R and is dissipated in the form of unwanted heat.
- The RC filter helps to reduce the ripple voltage, but it introduces output DC voltage losses when the load current is higher. Thus R-C filter is suitable only for light loads (small load current or large load resistance).





### b). π FILTER (C-L-C FILTER)

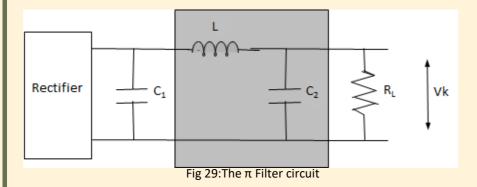


- π Filter act to overcome problems that generated by RC filter.
- · Resistor in RC filter is replaced with inductor (L).
- Inductor has lower reactance on d.c but has higher reactance to a.c.
- The first capacitor (C<sub>1</sub>) offers a low reactance to a.c component of rectifier output but provide more reactance to d.c components.
- Therefore, most of the a.c components will bypass through C1 and the d.c components flows through inductor (L).
- The capacitor C2 bypasses any other a.c component which the inductor had failed to block. As a result only the DC component appears across the load R<sub>L</sub>.





### c). LC FILTER

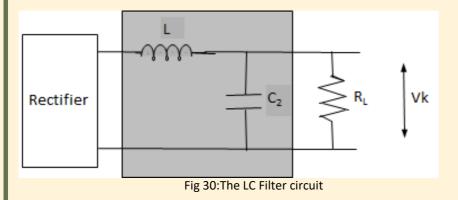


- · Combination of inductor and capacitor filter.
- An inductor is connected in series and a capacitor is connected in parallel to the load.
- · L gives low resistance to d.c but high reactance to a.c voltages.
- · Series inductor will reduce the ripples, when increasing the load current.
- Since the d.c resistance of the inductor is very low, it allows d.c current to flow easily through it.
- Capacitor appears open for d.c. So, all d.c components passes through the resistor RL.




PAGE 26

## REGULATOR

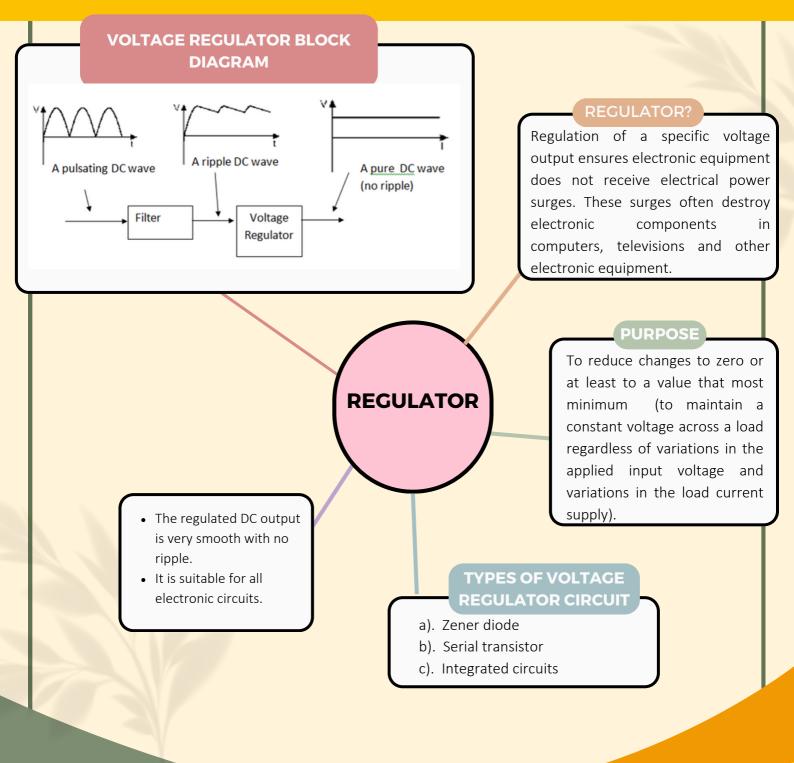

## REGULATOR

### a). ZENER DIODE'S VOLTAGE REGULATOR

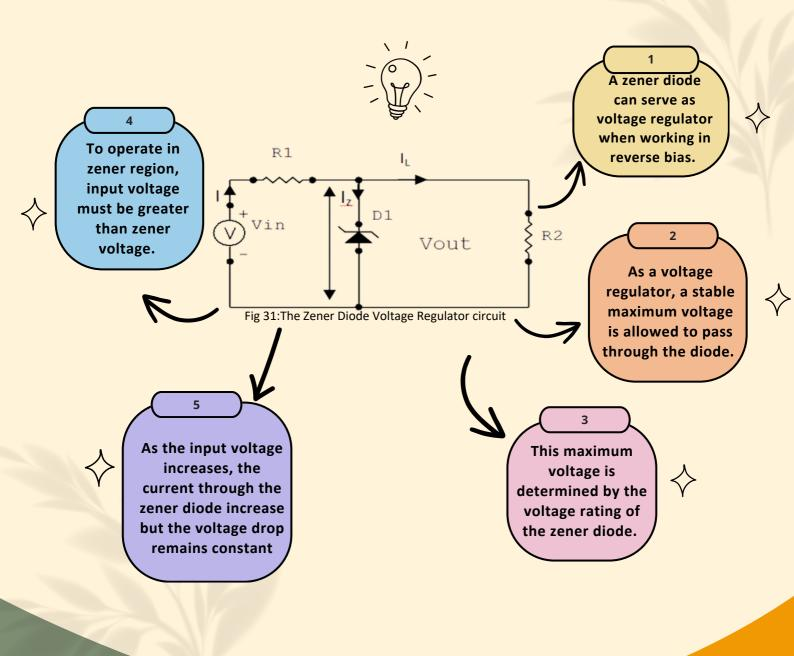



## REGULATOR

### b). SERIAL TRANSISTOR REGULATOR

### **ZENER DIODE**

Zener diodes is used as a reference voltage.

### i. When input voltage increase,

**OPERATION** 

constant current is delivered to a load as show in figure 32.

### SCHEMATIC DIAGRAM

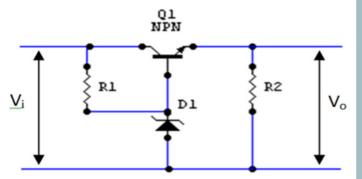


Fig 32:The Serial Transistor Regulator circuit

### **OPERATION**

Because of constant current at Base, constant current will deliver to load. A constant current value means output voltage is constant.

### OPERATION

ii. When input voltage increasing, zener voltage is constant but because R1 and Zener diode is serial, voltage drop across R1 is increasing too.

### **OPERATION**

iii. Zener diodes makes base voltage is constant and it will cause constant current flow through transistor and load.

PAGE 28

## REGULATOR

### c). INTEGRATED CIRCUIT REGULATOR

- A regulator has 3 terminals:
  - input
  - output
  - reference (common).

1 = INPUT 2 = GND / COM. 3 = OUT

- LM 78**XX** (where XX = 05,06, 08, 10, 12, 15, 18 or 24) was voltage regulator with three terminals as show in figure 33.
  - The XX value represents the output voltages.
  - For example, ouput of LM7805 = 5V and LM7812 = 12V.

123

Fig 33:The Intergrated Circuit Regulator

• The 78XX series are examples of positive output regulators. The output voltage show in table 2.

Table 2:The **78XX** series output voltage


Type Number 78XX	Output Voltag
7805	+5 V
7806	+6 V
7808	+8 V
7809	+9 V
7812	+12 V
7815	+15 V

#### Table 3: The 79XX series output voltage

Type Number 79XX	Output Voltage
7905	-5 V
7905.2	-5.2 V
7906	-6.0 V
7908	-8.0 V
7912	-12 V
7915	-15 V

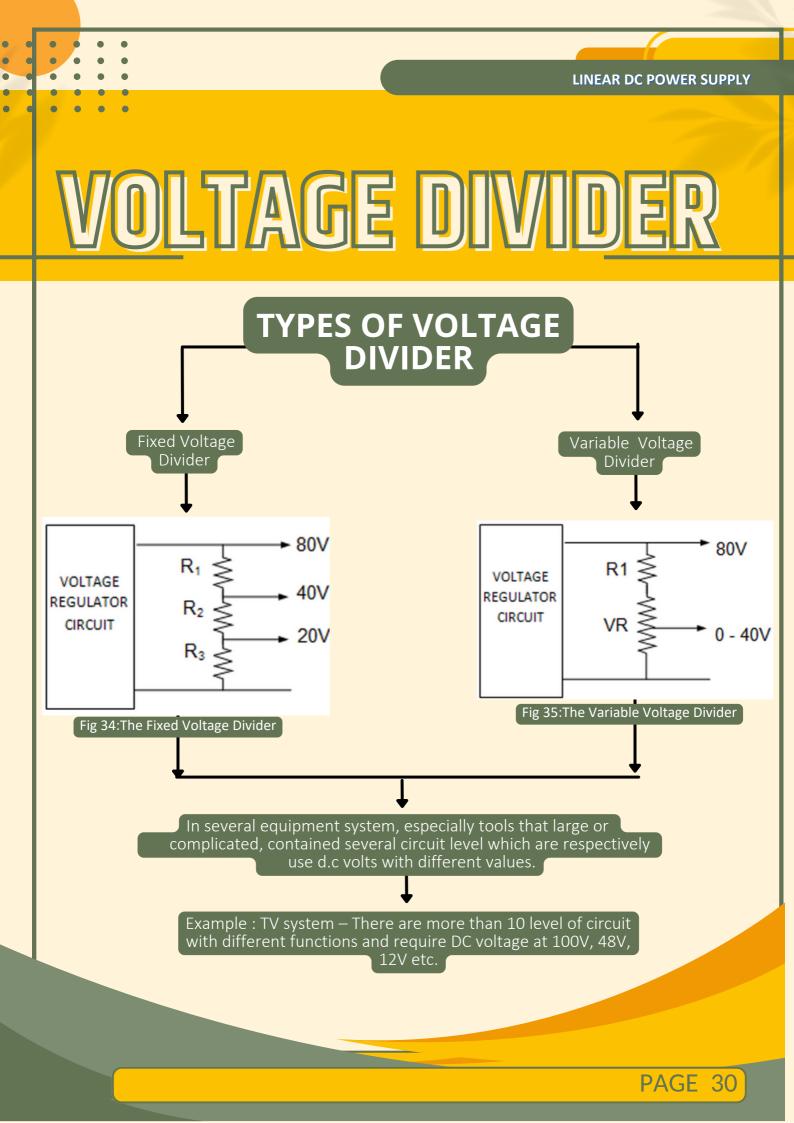The 79XX series are examples of negative output regulators. The output voltage show in table 3.





## EXERCISES

#### Question 1:

Describe the operation of the DC power supply block diagram which comprises these stages: transformer, rectifier, filter and voltage regulator.

#### **Question 2**

A power supply is a device that supplies electrical energy to one or more electric loads. It may also refer to devices that convert another form of energy (e.g. mechanical, chemical, solar) to electrical energy. Write the operation with aid of schematic diagram of a simple power supply. Includes your diagram with full wave rectifier,  $\pi$  filter and zener diode voltage regulator circuits.

### **Question 3**

State THREE (3) types of rectifier and briefly explain function of diode in rectifier circuit

#### **Question 4**

Sketch a schematic diagram of a simple power supply unit which includes of transformer, full- wave rectifier,  $\pi$  filter and serial transistor voltage regulator circuits.

#### **Question 5**

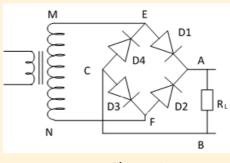


Figure 1

State the name of the rectifier circuit in figure 1 above and explain the operation during negative half of the input cycle.



## LINEAR DC POWER SUPPLY EXERCISES (OBJECTIVE)

1. In an unregulated power supply, if input a.c. voltage increases, the output voltage ......

A Increases

**B** Decreases

C Remains the same

D None of the above

2. A power supply which has voltage regulation of ..... is unregulated power supply

A. 0 %

B. 5 %

C. 10 %

D. 8%

3. An ideal regulated power supply is one which has voltage regulation of .....

A. 0%

B. 5%

C.10%

D. 1%

4. A Zener voltage regulator will cease to act as a voltage regulator if Zener current becomes

A. Less than load current

B. Zero

C. More than load current

D. None of the above

5. A Zener regulator \_\_\_\_\_ in the power supply

A. Increases the ripple

B .Decreases the ripple

C. Neither increases nor decreases the ripple

D. Data insufficient

6. The rectification is a process of converting \_\_\_\_\_

A. Alternating current into direct quantity

B. Alternating voltage into direct quantity

C. Alternating current or voltage into direct quantity

D. None of the above



### LINEAR DC POWER SUPPLY EXERCISES (OBJECTIVE) 7. Rectification can be done by using \_\_\_\_\_ A. Transformers **B.** Conductors C. Bridge rectifiers D. None of the above 8. The output of the rectification is \_\_\_\_\_ A. Unidirectional **B.** Bidirectional C. Multi-directional D. None of the above 9. The advantages of the traditional switching DC power supply are \_\_\_\_\_ A. Small size B. Light-weight C. Cost-effective D. All of the above 10. The efficiency of linear power supply is around \_\_\_\_\_ A. 10-20% B. 15-20% C. 30-40% D. 20-30%




## ANSWER

### Question 1

- Transformer To step up or step down the AC voltage. In a power supply unit, usually a step-down transformer is used to reduce the value of the input AC voltage to the required voltage of the electronic device
- Rectifier Is a circuit that converts the pulsating sinusoidal AC voltage to a pulsating DC voltage.
- Filter Is used to convert the pulse voltage to a ripple voltage. A filter circuit is a smoothing circuit that is used to obtain a smoother DC signal.
- Voltage Regulator Is used to reduce the voltage difference to zero. A voltage regulator helps to maintain constant output voltage.

### Question 2

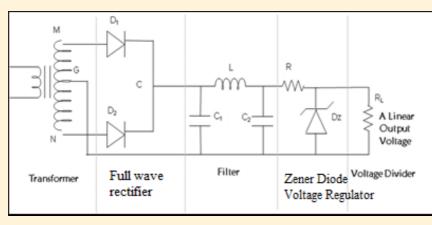


- Power supply circuits build using transformer, rectifier and filter. The addition parts are voltage regulator and voltage divider.
- Starting with an ac voltage, a steady dc voltage is obtained by rectifying the ac voltage, then filtering to a dc level and finally regulating to obtain a desired fixed dc voltage.

### Question 3

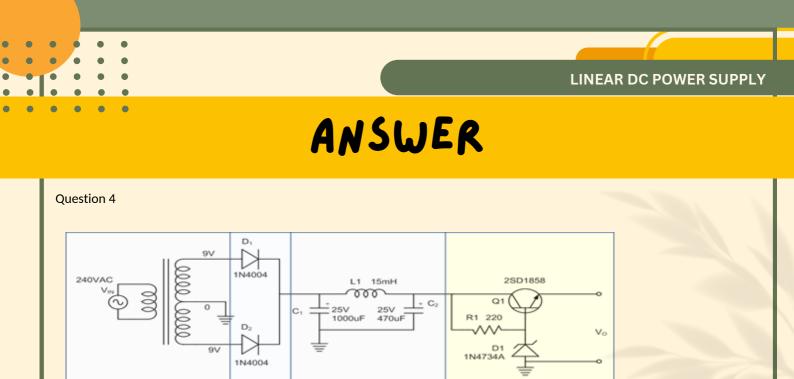i) Half-wave rectifierii) Full-wave rectifieriii) Bridge rectifier.

- Rectifier diodes are used to current flow in the circuit to a uni-direction. When diode is in forward bias condition, it will acts as a switch (close condition) and the current can pass through the circuit.
- But if diode is in reverse biased condition, it will acts as a switch (open condition) so the current can not
  pass through the circuit.





Filter

Voltage Regulator

Question 5 Bridge Rectifier Circuit

Transformer

Rectifier

### <u>Operation</u>

During the negative half of the input voltage cycle, M is negative and N is positive. D2 and D4 are forward biased, D1 and D3 are reversed biased. The direction will flow along N, F, A, B, C, E, M. A positive wave cycle will result at RL load. Since the direction current flow through RL is similar to the current flow through the positive cycles, so similar wave will be produced



PAGE 36

## ANSWER (OBJECTIVE)

- 1. A
- 2. C
- 3. A
- 4. B
- 5. B
- 6. A
- 7. C
- 8. A
- 0.7
- 9. D
- 10.C

### REFERENCES

Neal S. Widmer, Gregory L. Moss, Ronald J. Tocci (2017). Digital Systems-Principles and Applications (12th ed.). Pearson Higher Ed USA.

Malvino, A., & Bates, D. (2016). Electronic principles. New York:McGraw Hill Education.

Floyd, T. L. (2008). Electronic devices: Conventional current version. Upper Saddle River, NJ: Pearson Prentice Hall.

Paynter, R. T. (2006). Introductory electronic devices and circuits: Electron flow version. Upper Saddle River, N.J: Pearson Prentice Hall



